



VISVESVARAYA NATIONAL INSTITUTE OF
TECHNOLOGY, NAGPUR
Department of Electrical Engineering
Electronic Devices and Circuits (Code: ECL206)

Time: 1 hour

Sessional Examination I

Date: Sept 05, 2015
Time: 10:30–11:30 A.M.

Maximum Marks: 15
Weightage: 15 %

Important instructions:

- This is a closed book, closed notes examination.
- This question paper comprises total four questions printed on two pages.
- All the questions are compulsory.
- Maximum marks that can be obtained for a particular question are indicated on the right of the corresponding question.
- Non-programmable calculators are permitted for use during the examination.
- Please begin the answers to each main question on a new page of the answer booklet.
- Please indicate the important steps of reasoning/ calculations clearly.
- Unless otherwise specified, assume silicon semiconductor.
- The cut-in/ knee voltages for Si, Ge, and GaAs are 0.7 V, 0.3 V and 1.2 V respectively.
- Assume suitable data wherever necessary. Please mention the assumptions made, if any.

1. Answer the following. (No justification, No marks!)

(a) The depletion region penetrates more towards the lightly doped region. True or False?
Justify your answer. [1]

(b) The two types of capacitive effects found in *pn*-junction diode are _____. [1]


(c) At a certain temperature, the reverse saturation current for a *pn*-junction diode is found to be $25\mu A$. If the temperature is raised by an amount of $15^\circ C$, the new current is _____. [1]

2. Answer the following. (No justification, No marks!)


(a) For the circuit shown in Figure 2a, **Si** and **Ge** indicates silicon and germanium *pn*-junction diodes respectively. Find V_o . [1]

(b) For the circuit shown in Figure 2b, **Si1**, **Si2**, **Si3** indicates the silicon diodes. Find V_o and current through **Si1** [1]


(c) For the circuit shown in Figure 2c, V_i indicates the sinusoidal input signal with the peak-to-peak voltage as $2V_m$. Neatly sketch and label the corresponding V_o such that $V < |V_m|$. Assume the diode shown to be an ideal *pn*-junction diode. [1]

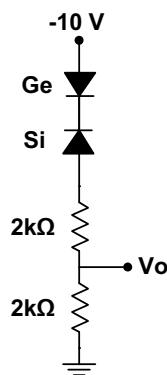

(a) Figure for Q.2a

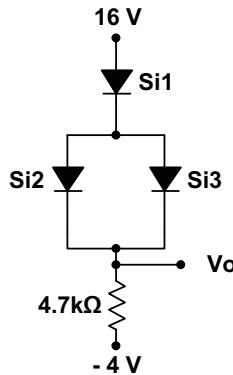

(b) Figure for Q.2b

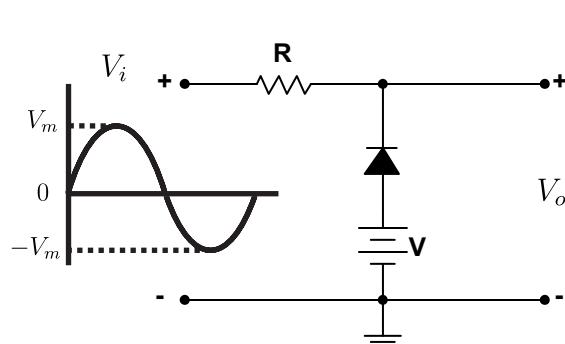

(c) Figure for Q.2c

Figure 2: Figures for Q.2

3. For the circuit shown in Figure 3, assume $\beta = 100$

- (a) Find if the transistor is in cutoff, saturation or active region. [1]
- (b) Calculate the percentage change in base current (I_B), collector current (I_C) and collector to emitter voltage (V_{CE}) when β is reduced to 50. [1]
- (c) Repeat Part (a) and Part (b) for $RE = 0\Omega$. [2]
- (d) What change is observed when RE is changed from $2\text{ k}\Omega$ to $0\text{ }\Omega$? Give proper explanation. [1]

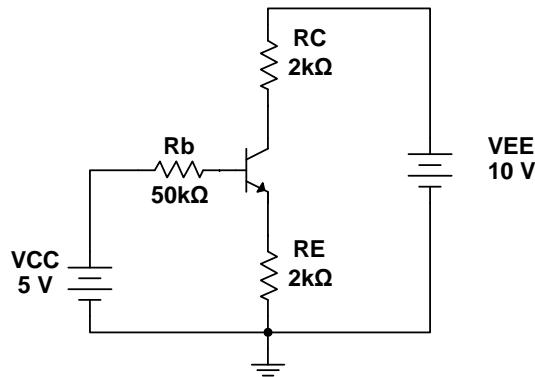


Figure 3: Figure for Q.3

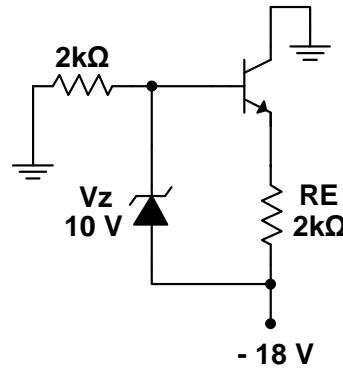


Figure 4: Figure for Q.4

4. For the circuit shown in Figure 4, assume transistor $\beta = 100$ and Zener breakdown voltage as 10 V .

- (a) Calculate transistor currents I_B , I_C , I_E [1]
- (b) Calculate V_{CE} [1]
- (c) Repeat Part (a) and Part (b) for $RE = 2\text{ }\Omega$. [2]

Q1

a] TRUE. To maintain/satisfy the charge neutrality principle, the number of uncovered charges on each side of a junction must remain equal.

- b]
- ① Transition / Depletion / space-charge capacitance.
 - ② Diffusion / storage capacitance.

c] Given : $(T_2 - T_1) = 15^\circ\text{C}$ if $I_1 = 25 \mu\text{A}$


$\therefore I_2 = I_1 \times 2^{\frac{(T_2 - T_1)}{10}}$

$$I_2 = 25 \mu\text{A} \times 2^{1.5} = 70.71 \mu\text{A}$$


As the reverse saturation current doubles every 10°C rise in Temp.

(2)

Q.2 a]

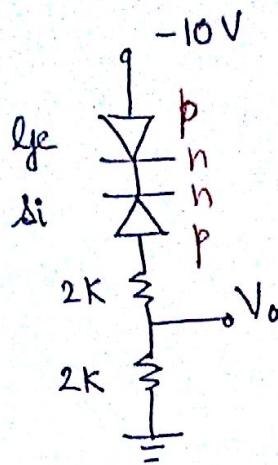


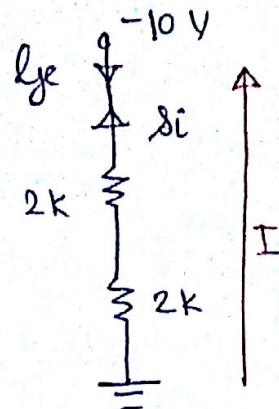Step ①: Determine the state of the diodes (ON/OFF)




Step ② :

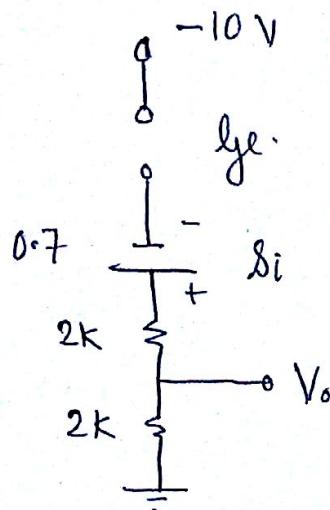Therefore, the Si diode will be replaced by 0.7V of Ge by an open circuit equivalents as shown.




As the current flowing is zero, no voltage is dropped across 2k resistor.


$$\therefore V_o = 0V$$

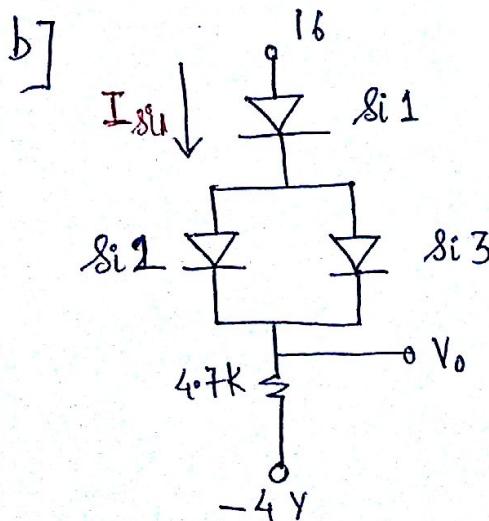

Step ①

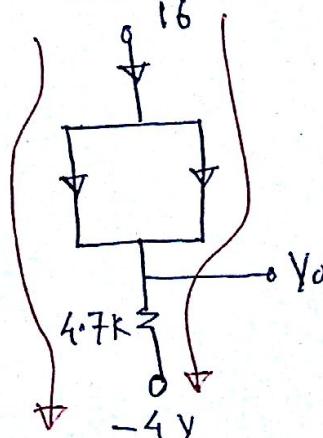

Step ②

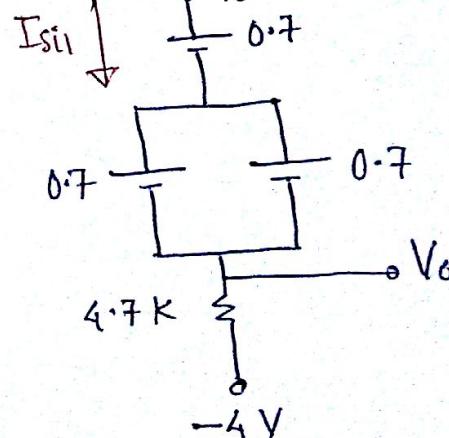

\therefore Applying KVL,


$$16 - 0.7 - 0.7 - 4.7k(I_{Si1}) + 4 = 0$$

$$\therefore I_{Si1} = 3.957 \text{ mA}$$

$$V_o = I_{Si1} \times 4.7k - 4 \therefore V_o = 14.6 \text{ V}$$

Q.2 c]

(3)

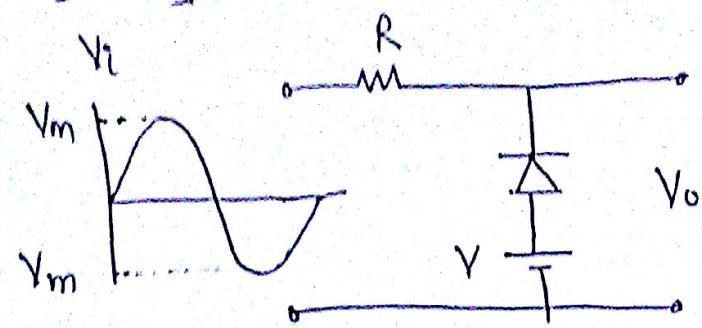


Step ① Determine the state of the diode.

Initially the diode is already forward biased.


The diode being ideal, acts as a short circuit, till the input

voltage reaches $V_i = V$. After which a constant voltage of V volts would be maintained, as shown, assuming $V < |V_m|$

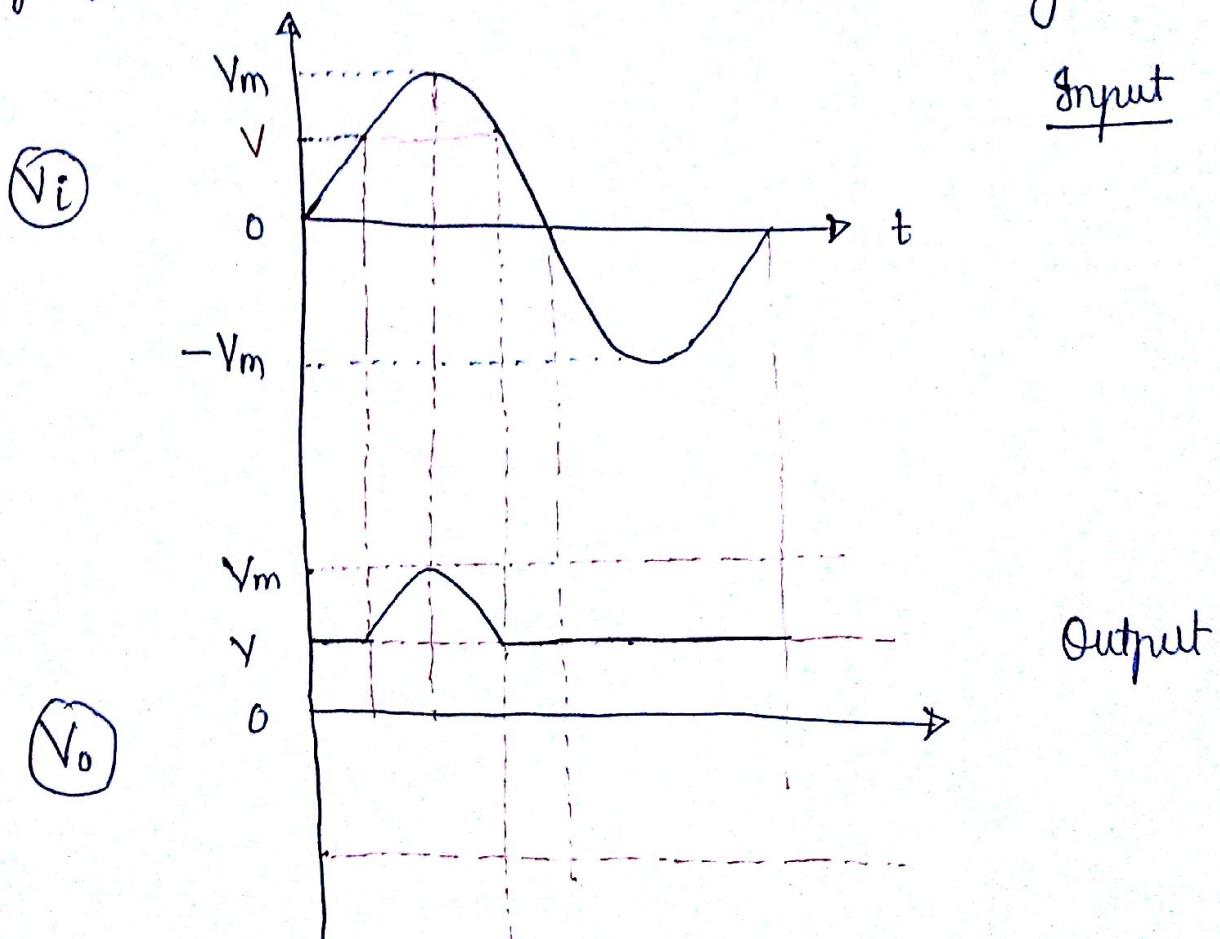

During the negative half cycle, the diode continues to remain in ON state (thus short circuit, ideally).

Q.3

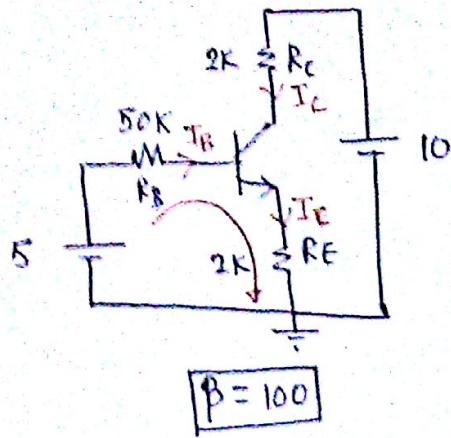


Determining the region of operation
of a transistor.

(4)

Region	Emitter Junction	Collector Junction
Active	Forward	Reverse
Saturation	Forward	Forward
Cutoff	Reverse	Reverse

For npn transistor:

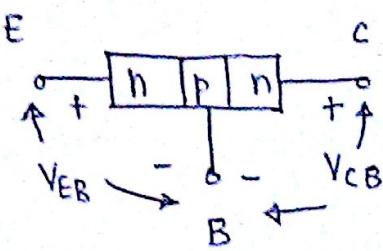

Region	V_{EB}	V_{CB}
Active	-ve	+ve
Saturation	-ve	-ve
Cutoff	+ve	+ve

(a) Step①: Calculate base current by applying KVL to base-emitter loop.

$$5 - 50k(I_B) - V_{BE} - I_E(2k) = 0$$

$$\therefore I_B = \frac{5 - 0.7}{50k + 101 \times 2k} \Rightarrow I_B = 17.063 \text{ mA}$$

Emitter Junction is forward bias i.e. $V_{BE} = +ve$ $| V_{EB} = -ve$
OR

$$\therefore I_C = \beta I_B \Rightarrow I_C = 1.7063 \text{ mA}$$

$$I_E = (1+\beta)I_B \Rightarrow I_E = 1.7234 \text{ mA}$$

Step ②: To check the Collector Junction, apply KVL along Collector-base junction.

$$10 - 2k(I_C) - V_{CB} + 50k(I_B) - 5 = 0$$

$$\therefore V_{CB} = 5 - 2k(100 \times I_B) + 50k(I_B)$$

$$\therefore V_{CB} = 2.453 \text{ V} \quad \text{i.e. POSITIVE}$$

The transistor
is in ACTIVE
REGION

(5)

* Verify : Calculate $I_{C\text{sat}}$,

$$I_{C\text{sat}} = \frac{10}{4K} = 2.5 \text{ mA}$$

As $I_C = 1.7 \text{ mA} < I_{C\text{sat}} = 2.5 \text{ mA}$

\therefore The Transistor cannot be in saturation.

To calculate V_{CE} , apply KVL in collector emitter loop.

$$10 - 2K(I_C) - V_{CE} - 2K(I_E) = 0$$

$\therefore V_{CE} = 3.1414 \text{ V}$

(b)

For $\beta = 50$, $I_B = \frac{5 - 0.7}{50K + (51) \times 2K} \Rightarrow I_B = 28.28 \mu\text{A}$

$I_C = 1.414 \text{ mA}$	$I_E = 1.4427 \text{ mA}$
--------------------------	---------------------------

$$V_{CB} = 5 - 2K(50 \times I_B) + 50K(I_B) \Rightarrow V_{CB} = 0.808 \text{ V}$$

POSITIVE

$$V_{CE} = 10 - 2K(I_C) - 2K(I_E)$$

$V_{CE} = 4.8346 \text{ V}$

$I_{C\text{sat}} = 2.5 \text{ mA}$

Comparison :

	$\beta = 100$	$\beta = 50$	% change
I_B	17.063 mA	28.28 μA	65.73 %
I_C	1.7063 mA	1.414 mA	20.67 %
V_{CE}	3.1414 V	4.8346 V	53.899 %
Status	Active	Active	-

Q.3

(6)

[c] (i) For $R_E = 0 \Omega$ & $\beta = 100$

\therefore The transistor is SATURATION

$$5 - 50k(I_B) - V_{BE} = 0 \Rightarrow I_B = \frac{5 - 0.7}{50k} \Rightarrow I_B = 86 \text{ mA}$$

$$I_C = 8.6 \text{ mA}$$

$$I_E = 8.686 \text{ mA}$$

$$I_{C\text{sat}} = 5 \text{ mA}$$

$$V_{CB} = 10 - 2k(I_C) + 50k(I_B) - 5 \Rightarrow V_{CB} = -7.9 \text{ V}$$

$$V_{CE} = 10 - 2k(I_C)$$

$$\therefore V_{CE} = -7.2 \text{ V}$$

(ii) For $R_E = 0 \Omega$ & $\beta = 50$

$$5 - 50k(I_B) - V_{BE} = 0 \Rightarrow I_B = 86 \text{ mA}$$

$$I_C = 4.3 \text{ mA}$$

$$I_E = 4.386 \text{ mA}$$

$$I_{C\text{sat}} = 5 \text{ mA}$$

$$V_{CB} = 10 - 2k(I_C) + 50k(I_B) - 5$$

$$V_{CB} = 0.7 \text{ V}$$

$$V_{CE} = 10 - 2k(I_C) \\ = 10 - 2k(4.3 \text{ mA})$$

$$V_{CG} = 1.4 \text{ V}$$


Region Comparison :

	$\beta = 100$	$\beta = 50$	% change
I_B	86 mA	86 mA	0 %.
I_C	8.6 mA	4.3 mA	100 %.
V_{CE}	-7.2 V	1.4 V	119.4 %.
Status	Saturation	Active	-

(d) For Fixed-bias configuration, change in β changes ($R_E = 0 \Omega$) the operation region.

For Emitter-bias configuration, change in β or ($R_E \neq 0 \Omega$) retains the operating region.

Q.4

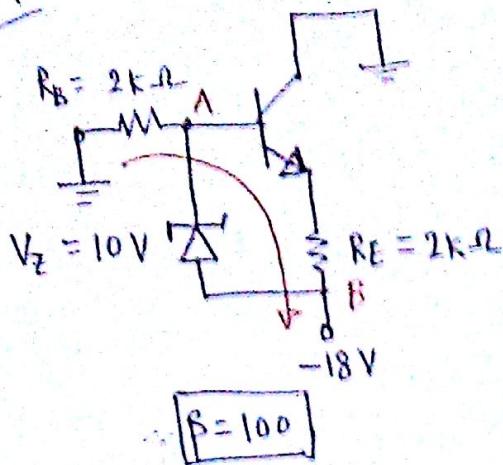

Step ① :

First determine if the Zener diode region of operation.

$$-2k(I_B) - 0.7 - 2k(I_E) + 18 = 0$$

$$-2k(I_B) - 0.7 - 2k(100 \times I_B) + 18 = 0$$

$$I_B = \frac{18 - 0.7}{2k + 100 \times 2k}$$

$$\Rightarrow I_B = 84.8 \mu\text{A} \quad I_E = 8.48 \text{ mA}$$

$$V_{AB} = V_{BE} + R_E \times I_E \Rightarrow V_{AB} = 0.7 + 2k(8.48 \text{ mA})$$

Step ② : Calculate actual values: $V_{AB} = 17.83\text{V}$

As $V_{AB} > V_Z$, the Zener goes into break-down maintaining

$$V_{AB} = 10\text{V} = V_Z$$

$$V_{RE} = 10 - 0.7 = 9.3\text{V}$$

$$I_E = \frac{9.3}{2k} \quad \therefore I_E = 4.65 \text{ mA}$$

$$\therefore V_{CE} = 2k(4.65 \text{ mA}) - 18 \Rightarrow V_{CE} = -8.7 \text{ V}$$

For $R_E = 2\Omega$: Step ①:

$$-2k(I_B) - 0.7 - 2(I_E) + 18 = 0$$

$$-2k(I_B) - 0.7 - 2(100 \times I_B) + 18 = 0$$

$$\therefore I_B = \frac{18 - 0.7}{2k + 100 \times 2} = \frac{18 - 0.7}{2k + 200} = \frac{17.3}{2.2k}$$

$$\therefore I_B = 7.86 \text{ mA} \quad I_E = 0.794 \text{ A}$$

$$V_{RE} = 2 \times 0.794 \Rightarrow V_{RE} = 1.58 \text{ V}$$

$$\therefore V_{AB} = 0.7 + 1.58 \Rightarrow V_{AB} = 2.28 \text{ V} \quad \therefore \text{Zener diode is OFF}$$

$$\therefore V_{CE} = V_{RE} - 18 \Rightarrow V_{CE} = -15.71 \text{ V}$$