



VISVESVARAYA NATIONAL INSTITUTE OF
TECHNOLOGY, NAGPUR
Department of Electrical Engineering
Electronic Devices and Circuits (Code: ECL206)
Semester-III

Slot: G
Date: Oct 10, 2015 (Sat)
Time: 10:30–11:30 A.M.

Time: 1 hour

Sessional Examination II

Maximum Marks: 15
Weightage: 15 %

Important instructions:

- This is a closed book, closed notes examination.
- This question paper comprises total four questions printed on two pages.
- All the questions are compulsory.
- Maximum marks that can be obtained for a particular question are indicated in the brackets [] on the extreme right of the corresponding question.
- Non-programmable calculators are permitted for use during the examination.
- Please begin the answers to each main question on a new page of the answer booklet.
- Please indicate the important steps of reasoning/ calculations clearly.
- Unless otherwise specified, assume silicon semiconductor.
- The cut-in/ knee voltages for Si, Ge, and GaAs are 0.7 V, 0.3 V and 1.2 V respectively.
- Typical h -parameter values for a transistor in common-emitter configuration are: $h_i = 1.1k\Omega$, $h_r = 2.5 \times 10^{-4}$, $h_f = 50$, and $h_o = 25\mu A/V$
- Assume suitable data wherever *necessary*. Please mention the assumptions made, if any.

1. Answer the following.

- (a) The three important temperature dependent parameters which are responsible for the change in collector current of a transistor are _____. [1]
- (b) For a fixed-biased transistor circuit, let the dc $V_{cc} = 20V$, $I_c = 1mA$ and $R_c = 1k\Omega$. If the thermal resistance θ is $500^\circ C/W$, the rate of variation of collector current with respect to the junction temperature i.e. $\frac{\partial I_c}{\partial T_j}$ is given as _____. [1]
- (c) For the circuit shown in Figure 1a, find the collector current I_{C2} flowing through the transistor Q_2 . Assume both the transistors to be identical and have $\beta = 100$. [1]
- (d) For the multi-stage transistor circuit shown in Figure 1b, determine the emitter current for transistor T_2 using dc-analysis. Assume β for both the transistors to be 100. [1]

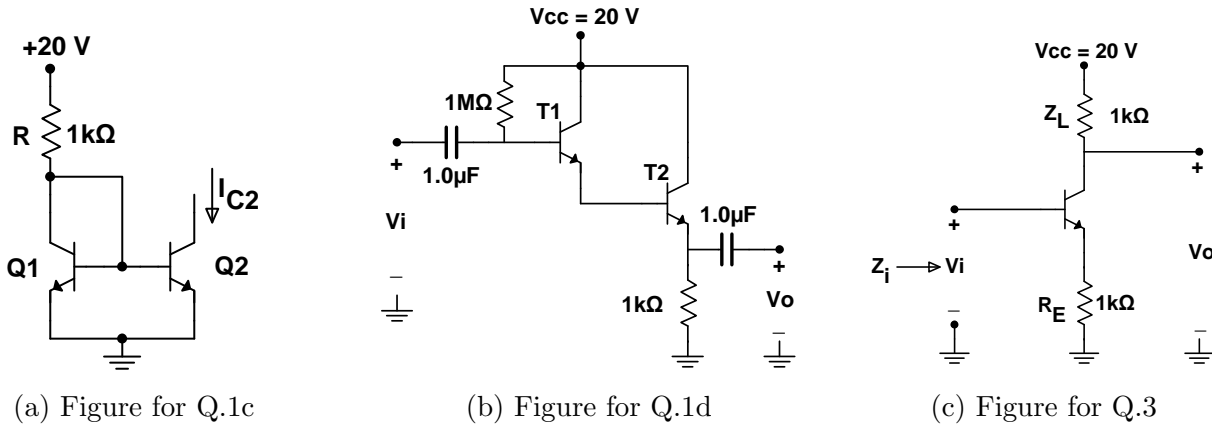


Figure 1: Figures for Q.1c, Q.1d, and Q.3

2. For the multi-stage transistor circuit shown in Figure 2

- Neatly draw and label the h -parameter model. (No labelling, no marks!) [1]
- Calculate the following for individual stages: (A_{I1} , Z_{i1} , A_{V1} , Z_{o1}) and (A_{I2} , Z_{i2} , A_{V2} , Z_{o2}). [3]
- Calculate overall (combined) gains (A_I , A_V) and impedances (Z_i , Z_o) (as shown by arrows). [2]

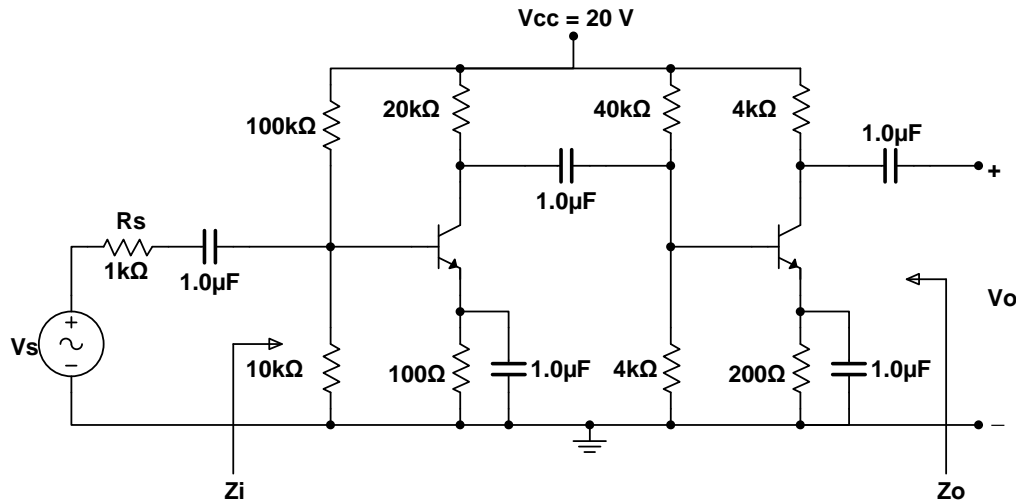


Figure 2: Figure for Q.2

3. For the circuit shown in Figure 1c, .

- Neatly draw and label the hybrid (h) equivalent for small-signal ac analysis. (No labelling, no marks!) [1]
- Calculate Z_i . (Hint: Apply Kirchhoff's laws to the h -model obtained in Part (a) to obtain the voltage the current ratio.) [4]

Q.1

(a) The three primarily important, temperature dependent parameters are

① V_{BE} (Base-to-Emitter voltage):


V_{BE} decreases at a rate of 2.5 mV (optional) per degree change in temperature

② I_{CBO}/I_{CO} (Reverse saturation current):

I_{CBO} doubles with every 10°C rise in temperature.

③ β (current gain):

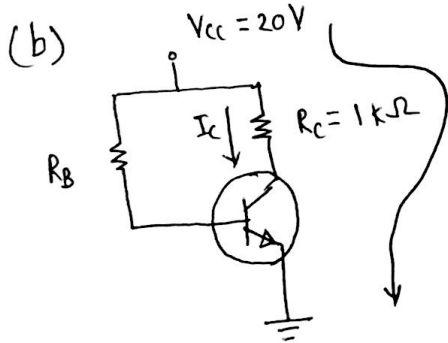Increases with an increase in the temperature.



$\theta = 500^\circ\text{C/W}$
 $I_C = 1\text{ mA}$; $R_C = 1\text{ k}\Omega$; $V_{CC} = 20\text{ V}$
 The thermal runaway equation is given by

$$\frac{\partial P_C}{\partial T_J} < \frac{1}{\theta}$$

$$\Rightarrow \frac{\partial P_C}{\partial I_C} \times \frac{\partial I_C}{\partial T_J} = \frac{1}{\theta} \quad \text{--- (1)}$$

Considering threshold value of

For $\frac{\partial P_C}{\partial I_C}$, $P_C = I_C V_{CE} \quad \text{--- (2)}$

By applying KVL at collector-emitter loop; $V_{CC} - I_C R_C - V_{CE} = 0$

$$\therefore V_{CE} = V_{CC} - I_C R_C \quad \text{--- (3)}$$

$$\therefore P_C = I_C (V_{CC} - I_C R_C)$$

$$\therefore P_C = I_C V_{CC} - I_C^2 R_C$$

$$\frac{\partial P_C}{\partial I_C} = V_{CC} - 2 I_C R_C$$


$$= 20 - 2 \times 1 \times 10^{-3} \times 1 \times 10^3 = 18$$

from (3) & (2)

From (1),

$$\frac{\partial I_C}{\partial T_J} = \frac{1/\theta}{18} = \frac{1}{500 \times 18}$$
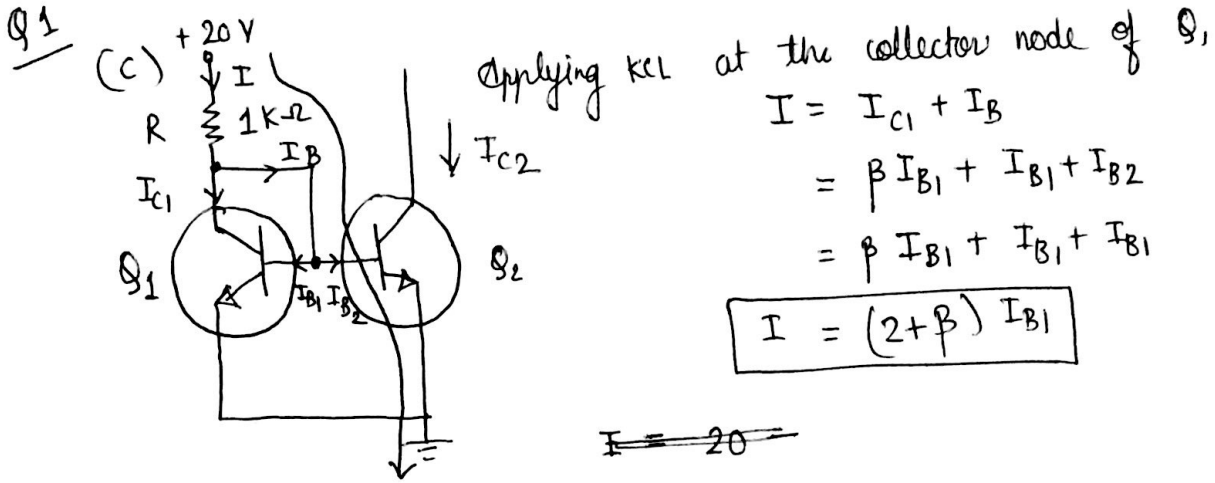
$$\frac{\partial I_C}{\partial T_J} = 0.111\text{ mA}/^\circ\text{C}$$



Applying KVL

$$20 - I \times 1k - 0.7 = 0 \Rightarrow I = \frac{20 - 0.7}{1k\Omega}$$

Assuming Silicon transistor

$$\therefore I = 19.3 \text{ mA}$$


$$\therefore I_{B1} = I_{B2} = \frac{19.3 \text{ m}}{(2 + \beta)} = 189.21 \mu\text{A}$$

$$\therefore I_{C2} = 18.92 \text{ mA}$$

Q.1

(a) ~~The given multistage transistor is of CC-CC configuration.~~

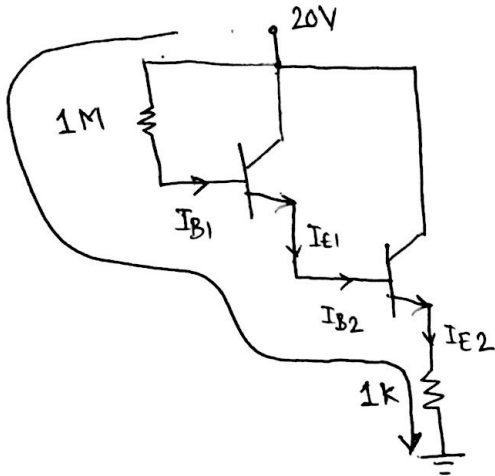(b) For dc-analysis open-circuit the capacitors



Applying KVL,

$$20 - 1M \times I_{B1} - 0.7 - 0.7 - 1k \times I_{E2} = 0$$

Now, $I_{E1} = I_{B2} = \cancel{\beta} I_{B1} (1 + \beta) I_{B1}$

$$I_{E2} = \cancel{\beta} I_{B2} (1 + \beta) I_{B2}$$

$$I_{E2} = (1 + \beta)(1 + \beta) I_{B1}$$


{ Darlington Pair

$$20 - 1M \times I_{B1} - 1.4 - 1k (101 \times 101) I_{B1} = 0$$

$$\therefore I_{B1} = \frac{20 - 1.4}{1M + 1k(10201)} = \cancel{1.66 \mu A} 1.66 \mu A$$

$$\therefore I_{E2} = 16.93 \text{ mA}$$

Q2 a]

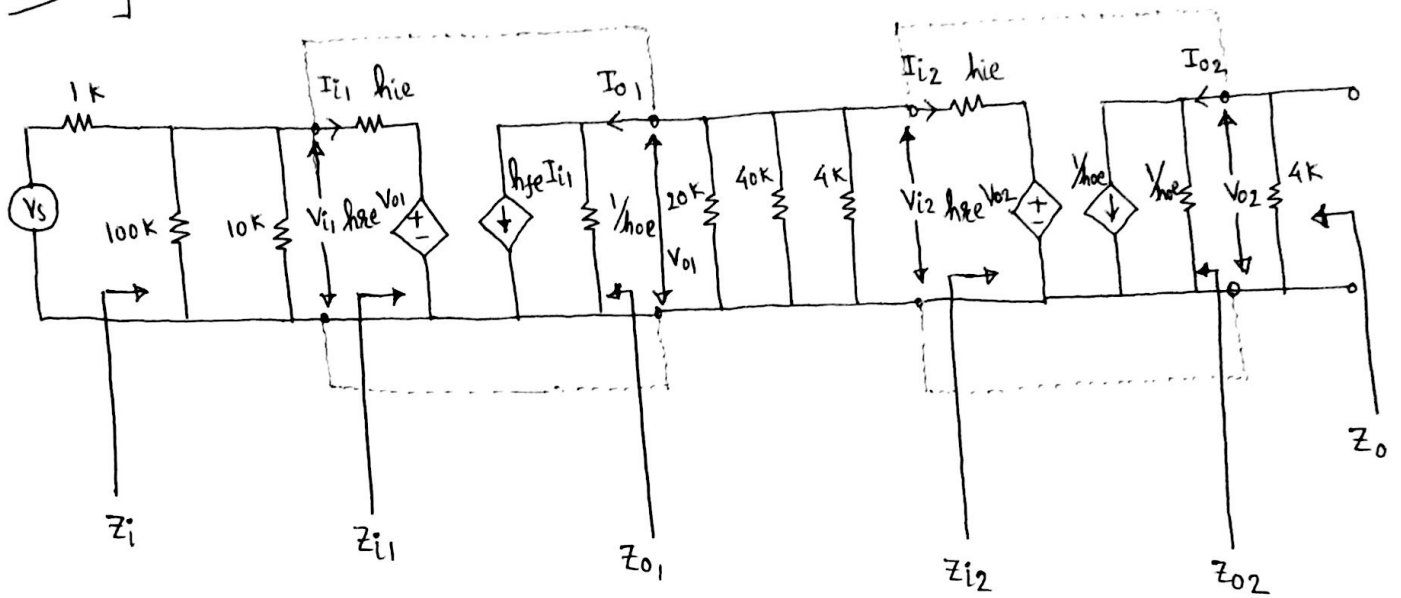

b] $h_{ie} = 1.1 \text{ k}\Omega$; $h_{re} = 2.5 \times 10^{-4}$; $h_{fe} = 50$; $h_{oe} = 25 \mu\text{A/V}$

Stage 2


$$A_{I2} = \frac{-h_{fe}}{1 + h_{oe}Z_{L2}} = -45.45$$

$$Z_{i2} = h_{ie} + h_{re}Z_{L2}A_{I2} = 1.05455 \text{ k}\Omega$$

$$A_{v2} = \frac{A_{I2} \times Z_{L2}}{Z_{i2}} = -172.39$$

77.

Stage 1

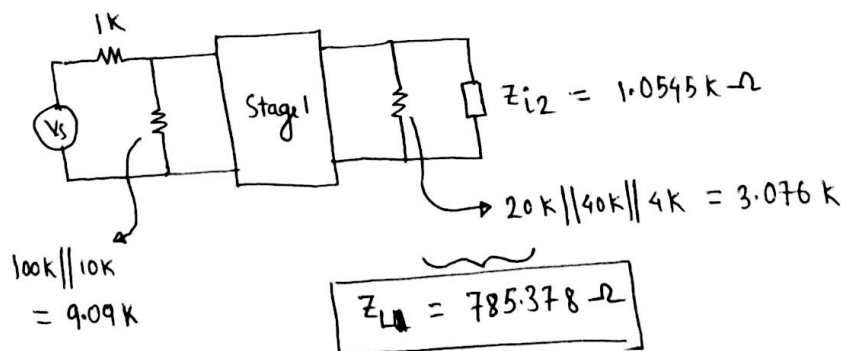

$$Z_{L1} = 20 \text{ k}\Omega \parallel 40 \text{ k}\Omega \parallel 4 \text{ k}\Omega \parallel Z_{i1} = 785.378 \Omega$$

$$R_{st} = 100 \text{ k}\Omega \parallel 10 \text{ k}\Omega \parallel 1 \text{ k}\Omega = 900.90 \Omega$$

$$A_{I1} = \frac{-h_{fe}}{1 + h_{oe}Z_{L1}} = \frac{-50}{1 + 25 \mu\text{A} \times 785.378} = -49.037$$

$$Z_{i1} = h_{ie} + h_{re}Z_{L1}A_{I1} = 1.090 \text{ k}\Omega$$

$$A_{V1} = \frac{A_{I1} Z_{L1}}{Z_{i1}} = \frac{-49.037 \times 785.378}{1.090 \text{ K}} \Rightarrow \boxed{A_{V1} = -35.33}$$

$$1/Z_{o1} = h_{oe} - \frac{h_{fe} h_{re}}{h_{ie} + R_{S1}} = 18.75 \mu\text{v}$$

$$\boxed{Z_{o1} = 53.325 \text{ k}\Omega}$$

Calculation of Z_{o2} : First calculate R_{S2}

$$R_{S2} = Z_{o1} \parallel 20\text{K} \parallel 40\text{K} \quad \cancel{R_{S2} = Z_{o1} \parallel Z_{L1} = 773.978 \Omega}$$

$$R_{S2} = Z_{o1} \parallel 20\text{K} \parallel 40\text{K} \parallel 4\text{K} = 2.909 \text{ k}\Omega$$



$$\therefore 1/Z_{o2} = h_{oe} - \frac{h_{fe} h_{re}}{h_{ie} + R_{S2}}$$

$$\boxed{Z_{o2} = 45.69 \text{ k}\Omega}$$

Combined Gains: $\frac{V_{o2}}{V_{i1}} = A_V = \underbrace{\frac{V_{o2}}{V_{i2}}}_{A_{V1}} \times \underbrace{\frac{V_{o1}}{V_{i1}}}_{A_{V2}}$ But $V_{i2} = V_{o1}$

Voltage gain
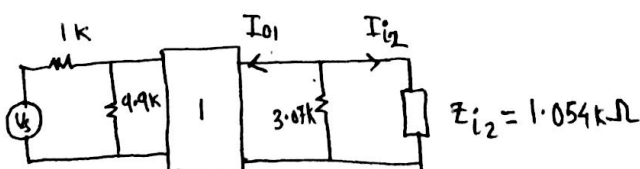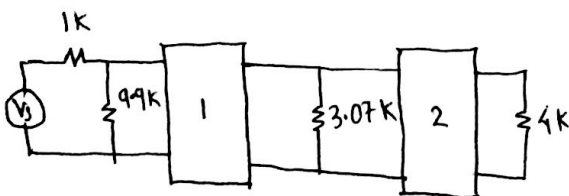
$$\therefore A_V = (-172.39) \times (-35.33) \Rightarrow \boxed{A_V = 6090.53}$$



Current Gain from intermediate

Stage:

$$A_{I_m} = \frac{I_{i2}}{-I_{o1}}$$

$$\text{But } I_{i2} = \frac{-I_{o1} \times 3.07\text{K}}{3.07\text{K} + 1.054\text{K}}$$

$$\therefore \frac{I_{i2}}{I_{o1}} = 0.74442 = A_{I_m}$$

$$A_I = A_{I1} \times A_{Im} \times A_{I2}$$

$$= -49.037 \times 0.7442 \times -45.45$$

$$\therefore \boxed{A_I = 1658.62}$$

$$Z_o = Z_{o2} \parallel 4k$$

$$\boxed{Z_o = 3.67 \text{ k}\Omega}$$


$$Z_i = 100k \parallel 10k \parallel Z_{i1}$$

$$\boxed{Z_i = 973.30 \Omega}$$

Comparison :

	Stage 1	Stage 2	Combined
A_I	-49.037	-45.45	1658.62
Z_i	1.090 k Ω	1.05455 k Ω	973.30 Ω
A_v	-35.33	-172.39	6090.53
Z_o	53.325 k Ω	45.69 k Ω	3.67 k Ω

Q3 (a)

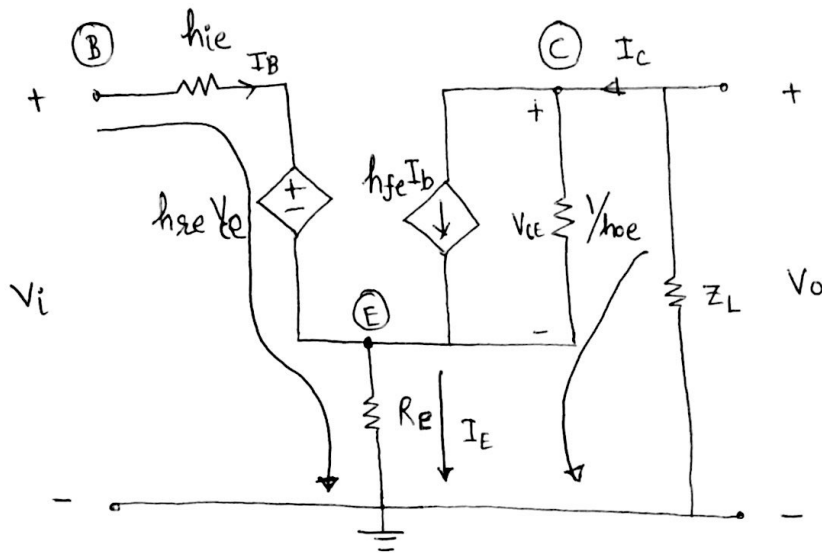

(b)

To obtain Z_i

$$Z_i = \frac{V_i}{I_B}$$

KCL at (E)

$$\left. \begin{aligned} I_E &= I_B + h_{fe} I_B + h_{oe} V_{CE} \\ I_E &= I_B (1 + h_{fe}) + V_{CE} h_o \end{aligned} \right\} \text{--- (1)}$$

Applying KVL at the input side,

$$V_i = h_{ie} I_B + h_{re} V_{CE} + R_E I_E = [h_{ie} + R_E (1 + h_{fe})] I_B + R_E V_{CE} h_o + h_{re} V_{CE}$$

Eliminating ~~V_{CE}~~ (expressing them in terms of I_B)

$$\therefore \text{Applying KVL at the output side, } V_i = I_B (h_{ie} + R_E (1 + h_{fe})) + V_{CE} \left(\frac{R_E h_o}{1 + h_{fe}} \right) \text{--- (2)}$$

$$-V_o = V_{CE} + I_E R_E$$

$$\text{But } -V_o = Z_L I_C = Z_L (h_{fe} I_B + h_{oe} V_{CE})$$

$$-(Z_L h_{fe} I_B + Z_L h_{oe} V_{CE}) = V_{CE} + I_E R_E$$

$$\text{From (1), } -Z_L h_{fe} I_B + Z_L h_{oe} V_{CE} = V_{CE} + I_B R_E (1 + h_{fe}) + V_{CE} h_{oe} R_E$$

$$\therefore V_{CE} \left(\frac{Z_L h_{oe}}{1 + h_{oe} R_E} + 1 \right) = I_B (R_E (1 + h_{fe}) + Z_L h_{fe})$$

$$\therefore V_{CE} = - \frac{I_B (Z_L h_{fe} + R_E (1 + h_{fe}))}{1 + h_{oe} (R_E + Z_L)}$$

Therefore,

$$\therefore V_{CE} = I_B \left(\frac{Z_L h_{fe} + R_E (1 + h_{fe})}{1 + h_{oe} (R_E + Z_L)} \right)$$

$$\& V_i = I_b \left(h_{ie} + R_E (1 + h_{fe}) \right) + V_{CE} \left(h_{re} + R_E h_{oe} \right)$$

$$\frac{V_i}{I_b} = h_{ie} + R_E (1 + h_{fe}) + (h_{re} + h_{oe} R_E) \left(\frac{Z_L h_{fe} + R_E (1 + h_{fe})}{1 + h_{oe} (R_E + Z_L)} \right)$$

$$\therefore \boxed{Z_i = \frac{V_i}{I_b} = h_{ie} + R_E (1 + h_{fe}) + (h_{re} + h_{oe} R_E) \left[\frac{Z_L h_{fe} + R_E (1 + h_{fe})}{1 + h_{oe} (R_E + Z_L)} \right]}$$

$$\therefore \boxed{Z_i = 49.67 \text{ k}\Omega}$$